

**— Computer Engineering —
Module 3: Combinatorial Circuits**



© 2018 Rehan Ahmed

M3 - 1



Modul 3: Combinatorial Circuits

- Formal Basics of Logics
 - Boolean Algebra
- Normalized and Minimized Forms
- Implementation of Combinatorial Circuits by Gates
- Design of Combinatorial Circuits
 - Minimization and KV Diagrams
 - Function Programming
- Delay Effects

© 2018 Rehan Ahmed

M3 - 2



Boolean Algebra Instantiated

- The **instantiated Boolean algebra** is defined explicitly by the following table:

Boolean Algebra	Instantiated
V	$\{0,1\}$
\emptyset	\vee
\otimes	\wedge
n	0
e	1
\bar{a}	\bar{a}

Alternative representations:

$a + b$ for $a \vee b$ or naming as "OR/ODER"
 $a \& b, ab$ for $a \wedge b$ or naming as "AND/UND"

© 2018 Rehan Ahmed


M3 - 3



Implementation of Logical Conjunctions (1)

- A technical implementation of logical conjunctions uses simple switching models instead of logical elements:

- AND:

 

- The light is only switched "on" (function's value equals 1), if the two switches are shut (a AND b equal 1), otherwise the light is switched "off" (function's value equals 0).


© 2018 Rehan Ahmed

M3 - 4



Implementation of Logical Conjunctions (2)

 - OR:
The light is switched "on", if the two switches are shut.



© 2018 Rehan Ahmed


M3 - 5



Boolean Algebra Instantiated (1)

- All conjunctions are represented in tables:

a	b	$a \wedge b$	a	b	$a \vee b$	a	\bar{a}
0	0	0	0	0	0	0	1
0	1	0	0	1	1	0	1
1	0	0	1	0	1	1	0
1	1	1	1	1	1		

 

© 2018 Rehan Ahmed

M3 - 6



Boolean Algebra Instantiated (2)

- Huntington Axioms:
 - H1: $a \vee b = b \vee a$
Commutative Law $a \wedge b = b \wedge a$
 - H2: $a \wedge (b \vee c) = (a \wedge b) \vee (a \wedge c)$
Distributive Law $a \vee (b \wedge c) = (a \vee b) \wedge (a \vee c)$
 - H3: $a \wedge 1 = a$
One Element $a \vee \bar{a} = 1$
 - H4: $a \wedge \bar{a} = 0$
Zero Element $a \vee 0 = a$

© 2018 Rehan Ahmed

M3 - 7

ifi

Boolean Algebra Instantiated (3)

- From those 4 Huntington's Axioms additional clauses are derived:
 - G1: $(a \wedge b) \wedge c = a \wedge (b \wedge c)$
Associative Law $(a \vee b) \vee c = a \vee (b \vee c)$
 - G2: $a \wedge a = a$
Idempotence Law $a \vee a = a$
 - G3: $a \wedge (a \vee b) = a$
Law of Absorption $a \vee (a \wedge b) = a$
 - G4: $\overline{a \wedge b} = \bar{a} \vee \bar{b}$
DeMorgan Law $\overline{a \vee b} = \bar{a} \wedge \bar{b}$ Also named as: NAND NOR


© 2018 Rehan Ahmed

M3 - 8

ifi

Boolean Expressions (1)

 - A Boolean expression is defined as a sequence of characters, which contains binary variables, the operators \wedge and \vee , and brackets, and which follows the syntactical rules, defined by the **syntax diagram**:



© 2018 Rehan Ahmed

M3 - 9

ifi

Boolean Expressions (2)

- Examples:
 - Syntactical correct expressions: $a \vee b, 0, (a \wedge b) \vee \bar{c}$
- No Boolean expressions, due to their syntactical **incorrectness**:
 - $a \vee a, 1, 0, () \vee c$
- For the Boolean Algebra instantiated the constants 0 and 1 are termed sometimes – closely related to statements – as **Boolean Truth Values**:
 - 0 : false 1 : true
- A Boolean expression by itself does not represent a Boolean value, since it may contain Boolean variables!
 - Only an assignment of a binary value with a Boolean value allows for the calculation of this Boolean expression's Boolean truth value

© 2018 Rehan Ahmed

M3 - 10

ifi

Representation of Boolean Functions

1. Function table, truth table ("Funktionstabelle")
2. Algebraic expression (symbolic form)
3. Graph

Function Table


a	b	f
0	0	0
0	1	0
1	0	0
1	1	1

Symbolic form

$$f = a \wedge b$$

Graph

(e.g., Shannon Tree)

 

© 2018 Rehan Ahmed

M3 - 11

ifi

Full Operators System (1)

- Definition:
 - A system of operators, with which all Boolean functions can be represented, is termed **full operators system**.
- The operators $(\wedge, \vee, \bar{\quad})$ do form such a **full operators system**.
- Example:
 - $a \leftrightarrow b$ equivalence with the same result as $(a \wedge b) \vee (\bar{a} \wedge \bar{b})$.
 - \leftrightarrow thus, replaced by basic operations $\wedge, \vee,$ and $\bar{\quad}$.

© 2018 Rehan Ahmed

M3 - 12

ifi

Full Operators System (2)

Operators System	Representation of ...		
	Negation	Conjunction	Disjunction
(\wedge, \vee, \neg)	\bar{a}	$a \wedge b$	$a \vee b$
(\wedge, \neg)	\bar{a}	$a \wedge b$	$\bar{a} \wedge \bar{b}$
(\vee, \neg)	\bar{a}	$\bar{a} \vee \bar{b}$	$a \vee b$
$(\bar{})$	$a \bar{}$	$(a \bar{} b) \bar{} (a \bar{} b)$	$(a \bar{} a) \bar{} (b \bar{} b)$
$(\bar{})$	$a \bar{}$	$(a \bar{} a) \bar{} (b \bar{} b)$	$(a \bar{} b) \bar{} (a \bar{} b)$
$(\wedge, \leftrightarrow)$	$a \leftrightarrow 1$	$a \wedge b$	$a \leftrightarrow b \leftrightarrow (a \wedge b)$

Hint: The operand " \wedge " may not be required in writing: $a \wedge b \leftrightarrow ab$

© 2018 Rehan Ahmed

M3 - 13



Tautology (1)

- In which cases two expressions A and B define the exact same Boolean function?
- Similarly noted as: Is $A \leftrightarrow B$ a tautology?
- Two Boolean functions are defined as follows:

$$f_1(a,b) = (a \wedge b) \vee (\bar{a} \wedge \bar{b})$$

$$f_2(a,b) = (a \vee \bar{b}) \wedge (\bar{a} \vee b)$$
- Is f_1 identical to f_2
or
is $(a \wedge b) \vee (\bar{a} \wedge \bar{b}) \leftrightarrow (a \vee \bar{b}) \wedge (\bar{a} \vee b)$ a tautology?

© 2018 Rehan Ahmed

M3 - 14



Tautology (2)

- Proof by utilizing (a) function tables or (b) logical transformations by applying algebraic laws.
 - (b) See next slide
 - (a) Two expressions are equivalent, if their results for all interpretations and, thus, all possible combinations of assignments for variables are identical.

a b	$(a \wedge b) \vee (\bar{a} \wedge \bar{b})$	$(a \vee \bar{b}) \wedge (\bar{a} \vee b)$	$A \leftrightarrow B$
00	1	1	1
01	0	0	1
10	0	0	1
11	1	1	1

© 2018 Rehan Ahmed

M3 - 15



Tautology (3)

- Transformations by applying algebraic laws:

$$\begin{aligned}
 (a \wedge b) \vee (\bar{a} \wedge \bar{b}) &= [(a \wedge b) \vee \bar{a}] \wedge [(a \wedge b) \vee \bar{b}] \\
 &\text{(Distributive Law)} \\
 &= [(a \vee \bar{a}) \wedge (b \vee \bar{a})] \wedge [(a \vee \bar{b}) \wedge (b \vee \bar{b})] \\
 &\text{(Distributive Law)} \\
 &= [1 \wedge (b \vee \bar{a})] \wedge [(a \vee \bar{b}) \wedge 1] \\
 &\text{(Inverse Element)} \\
 &= (b \vee \bar{a}) \wedge (a \vee \bar{b}) \\
 &\text{(Neutral Element)} \\
 &= (\bar{a} \vee b) \wedge (a \vee \bar{b}) \\
 &\text{(Commutative Law)}
 \end{aligned}$$

© 2018 Rehan Ahmed

M3 - 16



Modul 3: Combinatorial Circuits

- Formal Basics of Logics
 - Boolean Algebra
- Normalized and Minimized Forms
- Implementation of Combinatorial Circuits by Gates
- Design of Combinatorial Circuits
 - Minimization and KV Diagrams
 - Function Programming
- Delay Effects

© 2018 Rehan Ahmed

M3 - 17



Normal Forms

- A Boolean function may be represented by different Boolean expressions.
- A standardized representation of Boolean functions within a full operator's system such as $(\wedge, \vee, \bar{})$ is defined by the **conjunctive normal form (CNF)** – sometimes called "clausal normal form" – and the **disjunctive normal form (DNF)**.
- Definition:
 - A **literal** L_i is defined as either a positive variable x_i or its negation (negative variable) \bar{x}_i , thus, $L_i \in \{x_i, \bar{x}_i\}$
 - Only positive or negative literals exist!

© 2018 Rehan Ahmed

M3 - 18



Clauses (Product Terms)

Definition:

A **conjunctive clause (or product term)** $K(x_1, \dots, x_m)$ is defined as the **conjunction of literals**

$$\bigwedge_{i \in \{1, \dots, m\}} L_i = L_1 \wedge \dots \wedge L_m$$

or the constants "0" or "1"

Examples: $a \wedge a \wedge b$ $\bar{x}_i \wedge x_i$

Every conjunctive clause $K(x_1, \dots, x_m) = \bigwedge_{i \in \{1, \dots, m\}} L_i$ may be represented in a form such that a single variable x only appears at most once in one literal.

© 2018 Rehan Ahmed

M3 - 19



Literals and Clauses

If $L_h = x, L_j = x, h \neq j$ (multiple "positive" appearances)

$$\begin{aligned} \Rightarrow L_h \wedge L_j &= x \\ \Rightarrow K(x_1, \dots, x_m) &= \bigwedge_{i=1}^m L_i \end{aligned}$$

Multiple appearances of x can be reduced due to the Idempotence Law ($x \wedge x = x$).

If $L_h = x$ and $L_j = \bar{x}$ (mixed "positive" and "negated" appearances)

$$\begin{aligned} \Rightarrow L_h \wedge L_j &= 0 \\ \Rightarrow K(x_1, \dots, x_m) &= 0 \quad (\text{clause equals } 0) \end{aligned}$$

© 2018 Rehan Ahmed

M3 - 20



Implicant and Minterm

Definition:

A conjunctive clause $K(x_1, \dots, x_n)$ is termed **implicant** of a Boolean function $y(x_1, \dots, x_n)$, if $K \rightarrow y$

- K implies y (K is an implicant of y), if y also takes the value 1 whenever K equals 1
- I.e., for every assignment $B \in \{0, 1\}^n$ the following holds true: If $K(B) = 1, y(B) = 1$ holds as well.

Definition:

An implicant of a Boolean function $y(x_1, \dots, x_n)$ is termed **minterm**, if a literal of each variable x_i within the function y of implicants exists exactly once.

Examples

- Minterms of a Boolean function $y(x_1, \dots, x_4)$: $x_1 \wedge x_2 \wedge x_3 \wedge x_4$ or $x_1 \wedge \bar{x}_2 \wedge x_3 \wedge x_4$
- No minterms of the Boolean function $y(x_1, \dots, x_4)$: $x_1 \wedge x_2$ or $x_1 \wedge \bar{x}_2 \wedge x_3 \wedge x_4$

© 2018 Rehan Ahmed

M3 - 21



Disjunctive Normal Form

Definition:

Assuming a Boolean function $y(x_1, \dots, x_n)$, a Boolean expression is termed to be **disjunctive normal form (DNF)** of the function y , if it exists as a **disjunction of all minterms** K_i .

$$y = K_0 \vee K_1 \vee \dots \vee K_k, \quad k \leq 2^n - 1$$

- No two conjunctions K_i, K_j exist with $i \neq j$, such that they are equivalent
- Any Boolean expression is in its disjunctive normal form, iff it is either a single conjunctive clause or a series of conjunctive clauses joined by " \vee ".

Examples

- $f(a, b, c) = a b c \vee a \bar{b} c \vee a \bar{b} \bar{c}$ determines a valid DNF
- $f(a, b, c) = a b c \vee a \bar{b} c \vee a b \bar{c} \vee a \bar{b} \bar{c}$ does not determine a DNF, since
 - $a \bar{b}$ does not contain all variables
 - $a b c$ and $c a b$ are equivalent
 - $a (b c \vee \bar{b} \bar{c})$ does not define a "pure" conjunction

© 2018 Rehan Ahmed

M3 - 22



Implicat and Maxterm

Definition:

A disjunctive clause $D(x_1, \dots, x_n)$ is termed **implicat** of a Boolean function $y(x_1, \dots, x_n)$, if $D \rightarrow y$

- D implies y (D is an implicat of y), if y also takes the value 0 whenever D equals 0
- I.e., for every assignment $B \in \{0, 1\}^n$ the following holds true: If $D(B) = 0, y(B) = 0$ holds as well.

Definition:

An implicat of a Boolean function $y(x_1, \dots, x_m)$ is termed **maxterm**, if a literal of each variable x_i within the function y of implicats exists exactly once.

Examples

- Maxterms of the Boolean function $y(x_1, \dots, x_3)$:
 $x_1 \vee x_2 \vee x_3$ or $x_1 \vee x_2 \vee x_3$

© 2018 Rehan Ahmed

M3 - 23



Conjunctive Normal Form

Definition:

Assuming a Boolean function $y(x_1, \dots, x_m)$, a Boolean expression is termed to be **conjunctive normal form (CNF)** of the function y , if it exists as a **conjunction of all maxterms** D_i .

$$y = D_0 \wedge D_1 \wedge \dots \wedge D_k, \quad k \leq 2^m - 1$$

- No two disjunctions D_i, D_j exist with $i \neq j$, such that they are equivalent
- Any Boolean expression is in its conjunctive normal form, iff it is either a single disjunctive clause or a series of disjunctive clauses joined by " \wedge ".

Examples

- $f(a, b, c) = (a \vee b \vee c) \wedge (a \vee b \vee \bar{c}) \wedge (a \vee \bar{b} \vee c)$ determines a valid CNF
- $f(a, b, c) = (a \vee b \vee c) \wedge (a \vee \bar{b}) \wedge (c \vee a \vee b)$ does not determine a CNF, since
 - $a \vee \bar{b}$ does not contain all variables
 - $a \vee b \vee c$ and $c \vee a \vee b$ are equivalent

© 2018 Rehan Ahmed

M3 - 24



DNF and CNF

- Any function with n variables *may* show up to 2^n minterms and maxterms, respectively.
- Example: For $n = 3$ those read in full and complete:

	Minterm	Maxterm
0	$\bar{a} \bar{b} \bar{c}$	$a \vee b \vee c$
1	$\bar{a} \bar{b} c$	$\bar{a} \vee b \vee c$
2	$\bar{a} b \bar{c}$	$a \vee \bar{b} \vee c$
3	$\bar{a} b c$	$\bar{a} \vee \bar{b} \vee c$
4	$a \bar{b} \bar{c}$	$a \vee b \vee \bar{c}$
5	$a \bar{b} c$	$\bar{a} \vee b \vee \bar{c}$
6	$a b \bar{c}$	$a \vee \bar{b} \vee \bar{c}$
7	$a b c$	$\bar{a} \vee \bar{b} \vee \bar{c}$

© 2018 Rehan Ahmed

M3 - 25

ifi

“Reading” and Utilizing Normal Forms

- Every single **minterm** of a **DNF** equals one dedicated row in the functions table, which maintains always the **function's value 1**.
- Every single **maxterm** of a **CNF** equals one dedicated row in the functions table, which maintains always the **function's value 0**.
- Disjunctive and conjunctive normal forms determine **unique representations!**
 - Except for permutations, such as abc, acb, bac, bca, cab, or cba which are all equivalent.
- Functions represented by a single minterm only, determine for a single assignment only the function's value 1
 - Aside from the trivial null function, those functions show a minimal number of 1s!
- Functions represented by a single maxterm only, determine for a single assignment only the function's value 0
 - Aside from the trivial one function, those functions show a maximal number of 1s!

© 2018 Rehan Ahmed

M3 - 26

ifi

Example: DNF and CNF

A Boolean function is uniquely specified by listing all minterms and maxterms, respectively.

c b a	y	Minterms	Maxterms
0 0 0	1	$\bar{a} \bar{b} \bar{c}$	
0 0 1	0		$\bar{a} \vee b \vee c$
0 1 0	0		$a \vee \bar{b} \vee c$
0 1 1	1	$a b \bar{c}$	
1 0 0	1	$\bar{a} \bar{b} c$	
1 0 1	0		$\bar{a} \vee b \vee \bar{c}$
1 1 0	0		$a \vee \bar{b} \vee \bar{c}$
1 1 1	1	$a b c$	

$$\text{DNF: } y = (\bar{a} \bar{b} \bar{c}) \vee (a b \bar{c}) \vee (\bar{a} \bar{b} c) \vee (a b c)$$

$$\text{CNF: } y = (\bar{a} \vee b \vee c) (a \vee \bar{b} \vee c) (\bar{a} \vee b \vee \bar{c}) (a \vee \bar{b} \vee \bar{c})$$

© 2018 Rehan Ahmed

M3 - 27

ifi

Reminder of DNF and CNF

- Disjunctive and conjunctive normal forms determine **unique representations!**
 - Except for permutations, such as abc, acb, bac, bca, cab, or cba which are all equivalent.

Example: $y = a \bar{b} \vee c$

DNF: $y = \bar{a} \bar{b} c \vee \bar{a} b c \vee a \bar{b} \bar{c} \vee a \bar{b} c \vee a b c$

CNF: $y = (a \vee b \vee c) \wedge (a \vee \bar{b} \vee c) \wedge (\bar{a} \vee \bar{b} \vee c)$

© 2018 Rehan Ahmed

M3 - 28

ifi

Minimized Forms

- Goals**
 - Deriving shortest possible expressions for a given Boolean function
 - Implementing such a function at the lowest possible costs!
- Similarly to the disjunctive and conjunctive normal forms, so-called **minimal disjunctive normal forms** (“Disjunktive Minimalform”) and **minimal conjunctive normal forms** (“Konjunktive Minimalform”) exist.
- Multiple minimal disjunctive and conjunctive normal forms may exist for the same Boolean function
 - Example:
 - $y = a \bar{b} \vee b \bar{c} \vee \bar{a} c$ and
 - $y = a \bar{c} \vee \bar{b} c \vee \bar{a} b$
 define an identical function and both are minimal disjunctive normal forms

© 2018 Rehan Ahmed

M3 - 29

ifi

Deriving Minimized Forms

- In search of such a minimal disjunctive/conjunctive normal form the approach may become complex for functions with many variables
 - No “unique” or even optimal algorithm exists to find “the” normal form
 - Thus, sub-optimal solutions may be determined only by applying heuristics
- The minimization of forms operates in two steps
 - Step 1: Derive the set of implicants and implicats, respectively, for a given Boolean function f , while ensuring that the number of literals is kept as small as possible.
 - Step 2: Select from these sets of implicants and implicats, respectively, the smallest possible number of implicants and implicats, respectively, such that their disjunction and conjunction, respectively, determine this function f .
- Prerequisites for practical minimizations**
 - Application of full operators systems with one operator only!

© 2018 Rehan Ahmed

M3 - 30

ifi

NAND/NOR Conversion

- The $(\bar{\wedge})$ system (NAND System) and $(\bar{\vee})$ system (NOR System) are **full operators systems** (cf. before)
 - ⇒ Any disjunctive and conjunctive expression can be represented within the NAND and NOR System
- Conversion options in four different cases
 - Case 1: Function in disjunctive form $\Rightarrow (\bar{\wedge})$ system
 - Case 2: Function in disjunctive form $\Rightarrow (\bar{\vee})$ system
 - Case 3: Function in conjunctive form $\Rightarrow (\bar{\vee})$ system
 - Case 4: Function in conjunctive form $\Rightarrow (\bar{\wedge})$ system
- Why are exactly those conversions relevant?
 - ⇒ Much simpler implementation in hardware!
 - NANDs or NORs are very simple to be implemented as combinatorial circuits.

© 2018 Rehan Ahmed

M3 - 31

ifi

NAND Conversion (Example for Case 1)

- Assume a function f provided in disjunctive form
 - To be converted into $\Rightarrow (\bar{\wedge})$ system
- Conversion in two steps:
 - Step 1: Double negation of entire f
 - Step 2: Application of DeMorgan law
 - Resulting in an expression, which only contains NAND operators

© 2018 Rehan Ahmed

M3 - 32

ifi

Example: NAND Conversion

$$\begin{aligned}
 y &= \overline{\overline{a} b c \vee a \overline{b} c \vee a b \overline{c} \vee a \overline{b} \overline{c}} \\
 &= \overline{\overline{a} b c \vee a \overline{b} c \vee a b \overline{c} \vee a \overline{b} \overline{c}} \\
 &= \overline{a b c \wedge a \overline{b} c \wedge a b \overline{c} \wedge a \overline{b} \overline{c}} \\
 &= \text{NAND}_4(\text{NAND}_3(\overline{a}, b, c), \text{NAND}_3(a, \overline{b}, c), \\
 &\quad \text{NAND}_3(a, b, \overline{c}), \text{NAND}_3(\overline{a}, \overline{b}, c))
 \end{aligned}$$

$\text{NAND}_k(x_1, \dots, x_k)$ is defined as a k -ary function, for which:

$$\text{NAND}_k(x_1, \dots, x_k) = \begin{cases} 0 & \text{for } x_1 = \dots = x_k = 1 \\ 1 & \text{otherwise} \end{cases}$$

© 2018 Rehan Ahmed

M3 - 33

ifi

Example: NAND₂ Function

Representation of the NAND₂ function by the $\bar{\wedge}$ operator:

Problem:

Operators $\bar{\wedge}$ and $\bar{\vee}$ do not show an **associative characteristic**.

$$(x_1 \bar{\wedge} x_2) \bar{\wedge} x_3 \neq x_1 \bar{\wedge} (x_2 \bar{\wedge} x_3)$$

$$(x_1 \bar{\vee} x_2) \bar{\vee} x_3 \neq x_1 \bar{\vee} (x_2 \bar{\vee} x_3)$$

$$\text{NAND}_3(x_1, x_2, x_3) = \overline{x_1 \wedge x_2 \wedge x_3} = \overline{(x_1 \bar{\wedge} x_2) \bar{\wedge} x_3}$$

$$(x_1 \bar{\wedge} x_2) \bar{\wedge} x_3 = \overline{x_1 \wedge x_2 \wedge x_3} \neq$$

$$x_1 \bar{\wedge} (x_2 \bar{\wedge} x_3) = \overline{x_1 \wedge x_2 \wedge x_3}$$

© 2018 Rehan Ahmed

M3 - 34

ifi

Summary September 26, 2018

- Formal Basics of Logic
 - Boolean Algebra Instantiated
 - Huntington's axioms, Boolean laws, expressions, and functions
 - Full operators systems
 - Representation
 - Function's table (Truth Table), symbolic/algebraic form, Shannon tree (Graph)
- Normalized and Minimized Forms
 - Clause/product term and literal
 - Disjunctive Normal Form (DNF), unique
 - Implicant and minterm
 - Row of function table with function's value 1
 - Conjunctive Normal Form (CNF), unique
 - Implicant and maxterm
 - Row of function table with function's value 0
 - Minimal Conjunctive/Disjunctive Normal Form
 - Not unique, but "short" due to the use of "suitable" minterms and maxterms
 - NAND_x function

© 2018 Rehan Ahmed

M3 - 35

ifi

Modul 3: Combinatorial Circuits

- Formal Basics of Logics
 - Boolean Algebra
- Normalized and Minimized Forms
- Implementation of Combinatorial Circuits by Gates
- Design of Combinatorial Circuits
 - Minimization and KV Diagrams
 - Function Programming
- Delay Effects

© 2018 Rehan Ahmed

M3 - 36

ifi

Implementation of Combinatorial Circuits

General hierarchy

- Register transfer level: logic circuits as elements
 - Multiplexer, shift registers, algebraic adder, ... **Examples to come**
 - Gate level: logic gates **Just discussed in M3 theoretically, ✓ now briefly transferred into gates**
 - AND, OR, NAND, ...
 - Electronic switch level: Transistors
 - Electrical engineering basics **Example to come**
 - Layout level: Transistor technologies
 - Electrical engineering basics **Example mentioned in M1**
- Bottom-up ↑

© 2018 Rehan Ahmed

M3 - 37

ifi

Gate Level


- Full abstraction from any internal technical details of electrical engineering (almost)
- Full focus on logical behavior
 - Mapping of logic, Boolean functions onto circuits without knowledge of electrical engineering
- All circuits are represented in terms of symbols
- Algebraic and logic operators differ world-wide:
 - & different symbol for AND "∧"
 - ≥ 1 the output value equals 1, if at all ≥1-inputs a 1 is applied, thus, OR "∨"
 - ° different symbol for the negation "¬"
- Further different symbols and operators available on the Web.

© 2018 Rehan Ahmed

M3 - 38

ifi

 Symboles (DIN 40900 Teil 12, ANSI/IEEE-Standard 91-1984, IEC-Standard & US-Symbole)



All circuits of these types are termed **gate(s)**.


© 2018 Rehan Ahmed

M3 - 39

ifi

Exclusive OR Gate

 Simple gates are used to set-up hierarchically complex gates, which by themselves use (partially) dedicated symbols.




Exclusive OR (Antivalenz) composed out of five simpler gates. Applied to detect and determine the carry bit (Überlaufbit) in additions.

© 2018 Rehan Ahmed

M3 - 40

ifi

Equivalence Gate

 

Equivalence (Äquivalenz) composed out of five simpler gates.

© 2018 Rehan Ahmed

M3 - 41

ifi

Modul 3: Combinatorial Circuits

- Formal Basics of Logics
 - Boolean Algebra
- Normalized and Minimized Forms
- Implementation of Combinatorial Circuits by Gates
- Design of Combinatorial Circuits
 - Minimization and KV Diagrams
 - Function Programming
- Delay Effects

© 2018 Rehan Ahmed

M3 - 42

ifi

Design of Combinatorial Circuits (1)

- Any practical design of circuits need to address
 - Gates are "ideal", they generate heat to be diverted
 - Gates need space in terms of square micrometer [μm^2]
 - Gates show delay effects (see end of M3)
- Technical criteria
 - Power consumption, switching time, space, material, durability
 - Correct implementation with respect to static, dynamics (hazards see end of M3)
 - Constraints: #input lines, #output lines, maximal power of inputs/output
- Economic criteria
 - Effort for the design (salaries, simulations, data bases)
 - Effort of implementation (costs per gate, costs per square micrometer [μm^2])
 - Effort of operation (costs for tests, installation, maintenance at operation)

© 2018 Rehan Ahmed

M3 - 43

ifi

Design of Combinatorial Circuits (2)

- Border line between technical and economic criteria not always clear
 - Selected criteria may be contradictory
 - Enhancing reliability \Rightarrow Increased costs (redundancy, space, ...)
 - Lower design costs \Rightarrow Increased design costs
 - Higher density of functionality (less chips) \Rightarrow Increased design costs
- \rightarrow The design process has to determine alternatives and for a given problem the best possible compromise on functionality and costs has to be found and selected.
- Major goal: By respecting mandatory technical requirements to reach an economically favorable compromise such that overall full costs are minimized.

© 2018 Rehan Ahmed

M3 - 44

ifi

Minimization

- Basic assumption
 - Implementation of circuits in two stages
- Representation of function to be found, which minimizes the costs of its implementation, termed in its result as
 - Minimal form
- The approach to generate this minimal form is termed
 - Minimization
- Minimization works in three different ways
 - Algebraic approach
 - Graphical approach
 - Table-based approach
- Algebraic and graphical approaches only work up to 5 or 6 variables, otherwise humans loose the comprehensive view, thus, table-based (maps) approaches are applied thereafter

© 2018 Rehan Ahmed

M3 - 45

ifi

Reality Check

Minimization Task	Prime Terms	Selection
Number of variables ≤ 6	KV Diagram	KV Diagram Coverage Maps
Assuming DF(CF), in search of DMF(CMF)	Consensus Quine-McCluskey	Coverage Maps ("Überdeckungstabelle")
Assuming DF(CF) in search of DMF(CMF)	Nelson	Coverage Maps

Extended and powerful methods are accessible in selected literature (dedicated field)


© 2018 Rehan Ahmed

M3 - 46

ifi

Graphical Approach

 - KV Diagram (Karnaugh and Veitch)
 - Also termed Karnaugh map, Karnaugh diagram
- Rectangle, for which the right half is assigned to the variable a and the left half is assigned to \bar{a} :



KV diagram for a single variable

© 2018 Rehan Ahmed

M3 - 47

ifi

KV Diagram (1)

- Numbered fields into determine the index of this variable's assignment
 - Index equals minterms, with the value 1
- By adding the truth values 0 or 1 in each of the KV diagrams fields, the Boolean function is characterized uniquely
- A KV diagram defines an additional representation of Boolean functions, especially considered as an alternative to function tables
- Examples:




© 2018 Rehan Ahmed

M3 - 48

ifi

KV Diagrams (2)

 - KV diagrams for additional variables are defined via mirroring
 - Each additional variable doubles the number of possible assignments



© 2018 Rehan Ahmed

M3 - 49


ifi

KV Diagrams (3)

- Every field is uniquely identified by reading the edges' names
 - Field 11 is assigned to: $a b \bar{c} d$

- The index with every field defines the index of this field's assignment of variables, while all variables are marked in in alphabetically reverse order

- Field 11 = $1011_2 = d \bar{c} b a$

 

© 2018 Rehan Ahmed

M3 - 50

ifi

KV Diagrams — Set-up (1)

- Assuming that the function y is defined by a function table
 - Each row of that function table corresponds to a single field in the KV diagram
 - ⇒ For each row of the functions table the corresponding index will be determined and the function's value will be inserted

- Hint, to find all fields within the KV diagram:

- Include all input variables in alphabetically reverse order into the table
- In turn, the KV diagram can be completed according to their indices, which originate from the table's top to the table's bottom row

© 2018 Rehan Ahmed

M3 - 51

ifi


KV Diagrams — Set-up (2)

Example: $y = \bar{a} b \vee b c \vee \bar{a} \bar{b} c$

Function table:

Index	c	b	a	y
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

Resulting in KV diagram:

 

© 2018 Rehan Ahmed


M3 - 52

ifi

Characteristics of KV Diagrams (1)

- Key characteristic
 - Minterms located symmetrically to any center line differ only in a single variable

- Example:

 

Minterm 0 = $\bar{c} \bar{b} \bar{a}$
 Minterm 1 = $c \bar{b} \bar{a}$
 Minterm 4 = $c \bar{b} a$
 Minterm 3 = $c b \bar{a}$

© 2018 Rehan Ahmed

M3 - 53

ifi

Characteristics of KV Diagrams (2)


- Boolean algebra tells that terms differing in a single variable only may be minimized!

- Example:

$$a b c \vee a b \bar{c} = a b (c \vee \bar{c}) = a b$$

- Thus, the resulting term does not contain the variable c anymore!

 - In turn, minterms located symmetrically to any center line can be combined to a simpler term!



© 2018 Rehan Ahmed

M3 - 54

ifi

Definition: Prime Implicant and Selection


- An implicant p is defined as a **prime implicant**, if no implicant $q \neq p$ exists, which is implied by p .
 $\forall q: q \neq p \Leftrightarrow \neg(p \rightarrow q)$
 - i.e., p embraces the largest possible order (von größtmöglicher Ordnung).
- Proposition:**
 Every function can be represented as a disjunction of its prime implicants.
- Prime implicants are accessible from any KV diagram
 - Select "manually" the largest possible blocks of ones, such that each block contains 2^k fields
- Example (continued next slide):
 $f = \bar{a} \bar{b} c \vee a \bar{b} c \vee a b \bar{c}$

© 2018 Rehan Ahmed


M3 - 55

ifi

Example (1)

 

 4 minterms:
 $(\bar{a} \bar{b} c, a \bar{b} c, a b c, \bar{a} b c)$



3 prime implicants:
 first order implicants
 $(\bar{a} \bar{b}, a c, b c)$

But $(\bar{a} \bar{b}, b c)$ would be sufficient!

$$f = \bar{a} \bar{b} c \vee a \bar{b} c \vee a b c \vee \bar{a} b c$$

$$= \bar{a} \bar{b} \vee a c \vee b c = \bar{a} \bar{b} \vee b c$$



© 2018 Rehan Ahmed

M3 - 56


ifi

Example (2)


$f = \text{minterms } (0,2,4,5,6,7)$

  

 $g = \bar{a} b c$
 determines an implicant



$g = b c$
 determines an implicant

 

$g = \bar{a}$
 determines an implicant



© 2018 Rehan Ahmed

M3 - 57


ifi

Example (3)


$f = \text{minterms } (0,2,4,5,6,7)$

  

$g = b$
 does not determine an implicant

 

$g = c$
 determines an implicant

 

$g = \bar{a} \vee c$
 does not determine an implicant

(Impl.)


© 2018 Rehan Ahmed

M3 - 58

ifi

Alternatives for Functions' Implementations

- Implementation of **re-appearing** functions by two alternatives:
 - By multiplexers/demultiplexers
 - Memory circuits
- A **multiplexer (MUX)** defines a circuit with multiple inputs and one output, for which by n control lines one of the 2^n inputs is selected and switched to the single output
- Multiplexers are classified according to their size
 - 2^n -1 - Multiplexer (alternatively as a 1-out-of- 2^n -multiplexer)
- Example 1-out-of-4-multiplexer:

 

© 2018 Rehan Ahmed

M3 - 59

ifi

Multiplexer-based Functions' Implementation

- Traditionally, a multiplexer controls data flows
- Here, it is applied to implement Boolean functions
 - A 2^n -1 - multiplexer can implement Boolean functions with $n+1$ variables
- An **implementation table** defines the behavior
 - 2^n columns for possible assignments of n control lines
 - 2 rows for the negated (negative) and non-negated (positive) $(n+1)$ -st variable
- Content and assignment
 - The table contains all function's values depending on the input variables
 - Finally, each column is considered separately and gets assigned a 1-ary function $g \in \{0, 1, a, \bar{a}\}$, with which the input will be applied to according to the combination of all control variables

© 2018 Rehan Ahmed

M3 - 60

ifi


Example

Implementing function f with a multiplexer:

$$f = \bar{a}c \vee \bar{b}c \vee a b \bar{c}$$

Implementation table in case of the selection of b and c as control inputs:

cb	00	01	10	11
$a=0$	0	0	1	1
$a=1$	0	1	1	0
$f=$	0	a	1	\bar{a}

 


© 2018 Rehan Ahmed

M3 - 61

ifi

Demultiplexers/Decoders

 - A circuit, which maps a single input depending on those n control lines onto one of the 2^n outputs, is termed **demultiplexer**
- Example 1-out-of-4 Demultiplexer:



- Remarks
 - A demultiplexer offers an enable input e and n inputs s_i for a binary number, which is decoded at the 2^n outputs a_j
 - If the enable input $e=0$, all outputs are at 0, otherwise a 2-bit number is decoded
 - Example: By applying the number 2 ($s_1=1, s_0=0$), the output at $a_2=1$ and all other outputs remain with 0
- Thus, a demultiplexer is termed also **decoder**

© 2018 Rehan Ahmed

M3 - 62

ifi

Memory-based Functions' Implementation

- All circuits discussed so far, such as gates, multiplexers, or decoders, are defined by the function known in advance

→ **hardwired logic**

- However, circuits with multiple functions on board have to offer a higher flexibility to be adaptable to many application demands. Such an adaptation is termed **personalization** or **programming**

→ **micro-programmable logic**
(cf. M6 for CPUs)


© 2018 Rehan Ahmed

M3 - 63

ifi

Scheme of a Memory Cells

 Scheme of memory cells, in which arbitrary function tables can be stored into:




© 2018 Rehan Ahmed

M3 - 64

ifi

Organization of Memory Cells (1)

 

© 2018 Rehan Ahmed

M3 - 65

ifi

Organization of Memory Cells (2)

- The **input configuration** (Eingangssignale) determines the selection of a memory cell (addressing) and the value stored at this address will be offered at the **output configuration** (Ausgangssignale)
- The output configuration of the decoder determines those minterms of n input configurations (the rows of the function table)
- **Storing** the value 1 for a dedicated output configuration i means that this minterm is OR-connected to this i -th output; the value 0 indicates that this minterm will not be used

© 2018 Rehan Ahmed

M3 - 66

ifi

Memory Types (1)

- The personalization of memory distinguishes a set of various different memory types with different characteristics:
- ROM (Read Only Memory)
 - Memory circuits which can only be read during operation
 - Programming was performed only once initially at the vendor's side (mask-programmable ROMs)
 - Content of storage will remain unchanged for its entire lifetime

Memory Types (2)

- PROM (Programmable Read Only Memory)
 - Programmable ROMs, which are programmed by the user
 - Programming:
 - Melting of fusible links (microscopic small connectors)
 - Stored charge based on dedicated physical processes, which maintain the charge within the circuit over years

Memory Types (3)

- EPROM (Erasable Programmable Read Only Memory)
 - A user-programmable memory circuit, which can be erased by applying UV light and which may be re-programmed again
 - Very small quartz windows on top cover of circuit provide access
 - Memory circuits with electrical erasing options (higher voltage):
 - EEPROM: Electrically Erasable PROM
 - EAROM: Electrically Alternable ROM
 - Application for memories of digital cameras (Compact Flash, Memory Stick)

Memory Types (4)

- RAM (Random Access Memory)
 - Memory, which enables reads and writes during normal operation
 - A RAM will loose its programmed content once it will be decoupled from the power supply!
 - Different implementations:
 - Dynamic RAM (DRAM)
 - Static RAM (SRAM)

Comparison of RAM and ROM

- Key differences
 - RW: read/write
 - Access Times (AT) for R/W
 - Maintaining memory's content (operations OP) without power supply
 - Memory size (MS)

	ROM	PROM	EPROM	Flash-PROM	DRAM	SRAM
RW	R	R	R ((W))	R (W)	RW	RW
AT	+	+	+ / -	+ / -	++	+++
OP	+	+	+	+	-	-
MS	+	+	+	+	+	+

Programmable Logic Array (PLA)

- Up to now the entire function table was stored in memory cells, while the function was implemented by its DNF (disjunctive normal form)
- Instead, by applying the DMF (minimal disjunctive normal form) many functions can be implemented efficiently (fewer memory cells)
- PLA (Programmable Logic Array):
 - In comparison to ROMs PLAs do see as the input configuration prime implicants for covering the function, instead of minterms
 - The decoder used up to now will be replaced by an AND matrix

FPLA and PAL

- PLAs are being personalized during production (similar to ROMs)
- A user-programmable PLA with a fixed number of input configurations n , product terms k , and output configurations m is termed **Field Programmable Logic Array (FPLA)**
- Technical alternatives include PAL circuits, which did personalize already the AND matrix and the OR matrix at the time of production
- The role of PALs and FPLAs is determined by the demand for "similar" functions to be available in many devices, which may differ in their specific instantiations: reduction of costs, but no need to be fully flexible (programmable), but with fast operation

© 2018 Rehan Ahmed

M3 - 73


ifi

Example: Implementation via PAL

Assume that the functions f_1 and f_2 , already have been minimized:

$$f_1 = a \bar{b} \vee a c \quad \text{and} \quad f_2 = \bar{a} \bar{c} \vee a c \vee a b \bar{c}$$

 Their PAL implementation reads as follows:



© 2018 Rehan Ahmed

M3 - 74

ifi

Modul 3: Combinatorial Circuits

- Formal Basics of Logics
 - Boolean Algebra
- Normalized and Minimized Forms
- Implementation of Combinatorial Circuits by Gates
- Design of Combinatorial Circuits
 - Minimization and KV Diagrams
 - Function Programming
- Delay Effects

© 2018 Rehan Ahmed

M3 - 75

ifi

Delay Effects


- The discussion of gates assumed so far that any logical operation was performed idealistically!
- In reality, gates are implemented by transistors, resistors (Widerstände), and capacitors, which are visible on the circuit's layout level.
- Thus, a temporal signal curve for an implemented gate differs from its ideal Boolean signal curve!

© 2018 Rehan Ahmed

M3 - 76

ifi

 Realistic and Ideal Signal Curve (Inverter)



© 2018 Rehan Ahmed

M3 - 77

ifi

Realistic Characterization of Gates

- Realistic effects on the gate level have been modeled in different models and complexities
- A simple model is termed **Delay Model (Totzeitmodell)**
 - Only signal delays are considered, which exist due to gates and links
 - A **real gate** is modeled by:
 - An **ideal gate** without any delays and
 - A **delay element (Totzeitglied)** with a defined delay, which depends on the switching time of the gate's implementation
 - The temporal behavior of a binary variable following the delay element is identical as of before the delay element, however only delayed by the time τ

$$a(t) \text{ --- } \boxed{\tau} \text{ --- } b(t) = a(t - \tau)$$


© 2018 Rehan Ahmed

M3 - 78

ifi

 Example: Delay Model of the Inverter/Negator

- Such a simple model allows for an investigation and a principle understanding of delay effects, however, the model is still too idealistic for concrete system designs




© 2018 Rehan Ahmed

M3 - 79

ifi

Example: Application of the Inverter

Assume:

 


Both gates shall show a delay of 1 ns

© 2018 Rehan Ahmed

M3 - 80

ifi

Time Chart

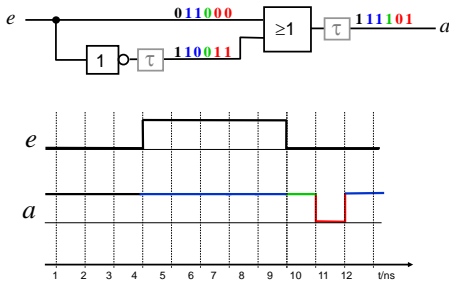

© 2018 Rehan Ahmed

M3 - 81

ifi

Behavior of Combinatorial Circuits

- Ideal combinatorial circuit**
 - The output configuration *does not change* in case of previous and current assignments at the input utilizing the same values
 - The output configuration *does change exactly once* in case of previous and current assignments at the input utilizing different values
- Realistic combinatorial circuit**
 - A change of the input configuration potentially results in different signal delays throughout the circuit
- Multiple changes of the output configuration, and thus the output signal curve, may occur until a stable final value is reached**
 - **Hazard (Hasardfehler)**


© 2018 Rehan Ahmed

M3 - 82

ifi

 Example

Function: $a = \bar{e}_1 e_2 \vee e_1 e_3$



© 2018 Rehan Ahmed

M3 - 83

ifi

Assumption: Change of Input

- The two following transitions (changes of input values) are considered:
 - Inputs e_2 and e_3 are constant at 1 and the input e_1 changes from 0 to 1
 - The inputs e_2 and e_3 are constant at 1 and the input e_1 changes from 1 to 0

© 2018 Rehan Ahmed

M3 - 84

ifi


Functional Evaluation

Function's values at the 2 transitions:

$$(e_3, e_2, e_1) = (1, 1, 0) \Rightarrow a = 1$$

$$(e_3, e_2, e_1) = (1, 1, 1) \Rightarrow a = 1$$

⇒ Correct behavior in these cases

 

For those transitions the value for a does not have to change under any circumstances, it needs to remain **constant 1** at all times


However, this behavior may not be guaranteed!

© 2018 Rehan Ahmed

M3 – 85

ifi

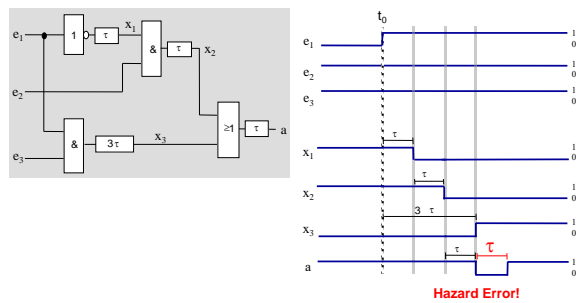Behavior Investigation Based on Delay Model




© 2018 Rehan Ahmed

M3 – 86

ifi

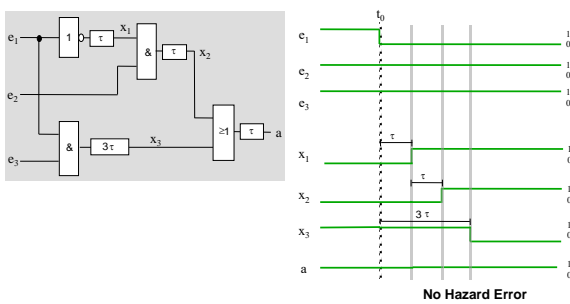Behavior Investigation Based on Delay Model



© 2018 Rehan Ahmed

M3 – 87

ifi

Result and Interpretation

- For a change of input e_1 from 0 to 1 the output signal curve does not remain constantly at the correct function's value
→ **Hazard Error**
- For a change of input e_1 from 1 to 0 the output signal curve is correct
→ **No worries!**
- Interpretation of this example's findings:
 - Functions may inherently carry a hazard (which is instantiated in terms of the hazard error), which may only become visible if dedicated input changes are applied
 - Thus, incorrect behaviors may occur such that output values may change, although ideally that should not happen
 - Does a suitable mechanism exist (a) to find out, if a hazard error may occur and if so (b) to solve this problem in a realistic manner?

© 2018 Rehan Ahmed

M3 – 88

ifi

Terminology Definitions

- A **change of input(s) (Eingabewechsel)** is defined as the change of one or multiple input configurations at a defined point in time
 - In case of a required change of multiple input configurations, these have to happen at the same point in time
- A **transition (Übergang)** determines the behavior of the combinatorial circuit, which is driven by the change of input(s).
 - A transition starts at the time the input configuration changes and ends at the time the circuit has reached its static state (Ruhezustand)
- A **hazard error** is defined as multiple changes of an output configuration within a single transition
 - Cf. example in blue above
- A **hazard** is defined as the logical-structural prerequisite for a hazard error, while no detailed delay values for gates implementing the function are considered

© 2018 Rehan Ahmed

M3 – 89

ifi

Hazard-afflicted Transitions


- Each hazard is a characteristic of one transition
- A hazard-afflicted transition is determined by
 - Logical function this combinatorial circuit implements
 - The structure of the same in terms of #gates and order of those (no delays)
- Given a combinatorial circuit and a transition, which ends up to be hazard-afflicted, the circuit contains a hazard
Hazard error → Hazard
- The inverse is not correct: The existence of a hazard-afflicted transition does not lead necessarily to a hazard error
Hazard ∧ unfavorable delay values → Hazard error

© 2018 Rehan Ahmed

M3 – 90

ifi

Example

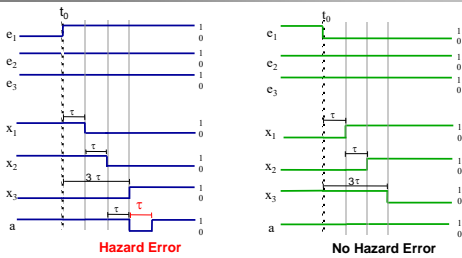

Transition $(e_3, e_2, e_1) : (1,1,0) \rightarrow (1,1,1)$ is hazard-afflicted, since the potential to show a hazard error exists!

© 2018 Rehan Ahmed

M3 - 91

ifi

Functional and Structural Hazards

- A **functional hazard** is a hazard, which originates from the function itself
 - Functional hazards always appear in any alternative combinational circuit implementing this function. It cannot be circumvented as such
 - Given an implementation as a combinational circuit, a suitable selection of delay values can prevent the functional hazard error to occur, but not the hazard itself
- A **structural hazard** is a hazard, which originates from the structure of the implemented circuit
 - Structural hazards can always be circumvented by developing an alternative combinational circuit with a different structure
 - Thus, the selection of a different minimal disjunctive/conjunctive normal form for that function solves the problem in full


© 2018 Rehan Ahmed

M3 - 92

ifi

Static 0-Hazard and 1-Hazard

 - Compared to transitions, hazards are either dynamic or static
- A hazard within a static 0-transition is termed **static 0-hazard**
 - Examples
- A hazard within a static 1-transition is termed **static 1-hazard**
 - Examples



The transition $(1,1,0) \rightarrow (1,1,1)$ within the previous example contains a static 1-hazard


© 2018 Rehan Ahmed

M3 - 93

ifi

Dynamic 01-Hazard and 10-Hazard

 - A hazard within a dynamic 01-transition is termed **dynamic 01-hazard**
 - Examples
- A hazard within a dynamic 10-transition is termed **dynamic 10-hazard**
 - Examples




© 2018 Rehan Ahmed

M3 - 94

ifi

Classifications of Hazards and Examples

 

Static 1-transition:

Transition (e_3, e_2, e_1) : $(1,1,0) \rightarrow (1,1,1)$

Dynamic 01-transition:

Transition (e_3, e_2, e_1) : $(0,1,1) \rightarrow (1,0,1)$

Dynamic 10-transition

Transition in inverse direction: $(1,0,1) \rightarrow (0,1,1)$

© 2018 Rehan Ahmed

M3 - 95

ifi